

MIPS based MCU Architecture

Final Project Assignment Definition

Hanan Ribo

08.07.25

Table of contents

| | | |
|-----|--|----|
| 1. | Aim of the project..... | 3 |
| 2. | Definition and prior knowledge..... | 3 |
| 3. | Assignment definition..... | 3 |
| | I/O devices connected: | 4 |
| 4. | Required Support of CPU Peripherals..... | 6 |
| 5. | Interrupt Service BUS Protocol of a Single Cycle CPU: | 13 |
| 6. | Pin Planner..... | 14 |
| 7. | Host Interface (to ITCM and DTCM) | 14 |
| 8. | Compiler, Simulator and Memory | 14 |
| 9. | CPU and MCU Test..... | 14 |
| 10. | MCU and PC communication using RS-232 interface (= Bonus)..... | 15 |
| 11. | Requirements | 15 |
| 12. | Grading policy | 17 |
| 13. | References..... | 17 |

1. Aim of the project

- Design, synthesis, and analysis of a simple (single cycle architecture) MIPS CPU core with Memory Mapped I/O, interrupt capability, and *Serial communication peripheral (entitles to a 20% bonus)*
- *Pipelined MIPS CPU core* instead of a single-cycle core (*entitles to a 10% bonus*)
- Understanding of CPU vs. MCU concepts, and FPGA embedded memory structures

2. Definition and prior knowledge

The aim of this project is to design CPU MIPS based MCU. The CPU will use a Single Cycle MIPS architecture and must be capable of performing full instruction set of simple MIPS (given as an appendix). The design will be located on Altera Board. The MIPS architecture is Harvard architecture in order to increase throughput and simplify the logic. For additional information regarding MIPS CPU, Architecture, ISA and instructions see MIPS technical documentation [1].

3. Assignment definition

The architecture must include a MIPS ISA compatible CPU with data memory DTCM and program memory ITCM for hosting the program data and code segments. The block diagram of an architecture is given in Figure 1. The CPU will have a standard MIPS register file. The top level and the MIPS core must be structural. The design must be compiled and loaded to the Altera board for testing. A single clock (CLK) should be used in the design.

Note: use push-button KEY0 as a System RESET (brings the PC to the first program instruction)


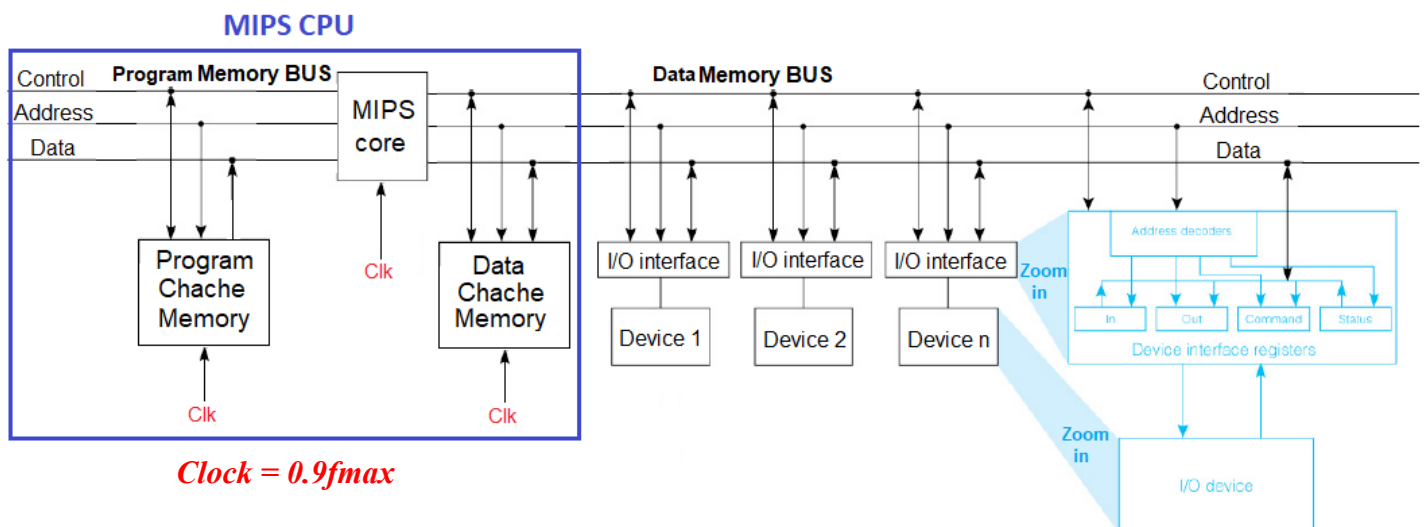


Figure 1 : MCU System architecture

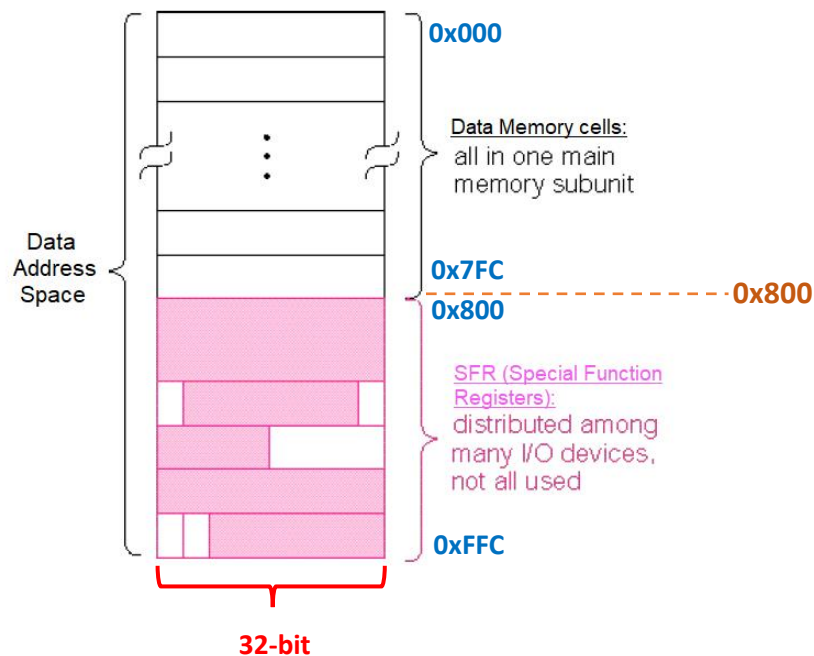- The GPIO (General Purpose I/O) is a simple decoder with buffer registers mapped to data address (Higher than data memory) as given in the assembly code examples that enables the CPU to output data to GPIO devices as LEDs and 7-Segment and to read the Switches array value.



The Data Address Space is 32-bit WORD aligned where the physical address space it is the lowest 12-bit $0 \dots 0A_{11} \dots A_0$ with partial mapping.

Figure 2: Data Address Space contains Data Memory and Memory Mapped I/O

I/O devices connected:

In the hardware test case, you will have to test an **ALU digital system** onto D10-Standard FPGA board.

- Board **ten** switches (SW9-SW0) and push **four** debounced pushbuttons (KEY3-KEY0) will be used as **Input interface**.
- Board **10** red LEDs (LEDR9-LEDR0) and **six** 7-segment displays (HEX5-HEX0) used as **Output interface**.
- Connections between the 2x20 GPIO Expansion Header and Cyclone V SoC FPGA

[Figure 2a: I/O interface of the DE10-Standard FPGA board](#)

[Figure 2b: I/O interface of the DE2-115 FPGA board](#)

```
#-----
#
#           MEMORY Mapped I/O
#-----
#define PORT_LED0[7-0] 0x800 - LSB byte (Output Mode)
#----- PORT_HEX0_HEX1 -----
#define PORT_HEX0[7-0] 0x804 - LSB byte (Output Mode)
#define PORT_HEX1[7-0] 0x805 - LSB byte (Output Mode)
#----- PORT_HEX2_HEX3 -----
#define PORT_HEX2[7-0] 0x808 - LSB byte (Output Mode)
#define PORT_HEX3[7-0] 0x809 - LSB byte (Output Mode)
#----- PORT_HEX4_HEX5 -----
#define PORT_HEX4[7-0] 0x80C - LSB byte (Output Mode)
#define PORT_HEX5[7-0] 0x80D - LSB byte (Output Mode)
#-----
#define PORT_SW[7-0] 0x810 - LSB byte (Input Mode)
#-----
```

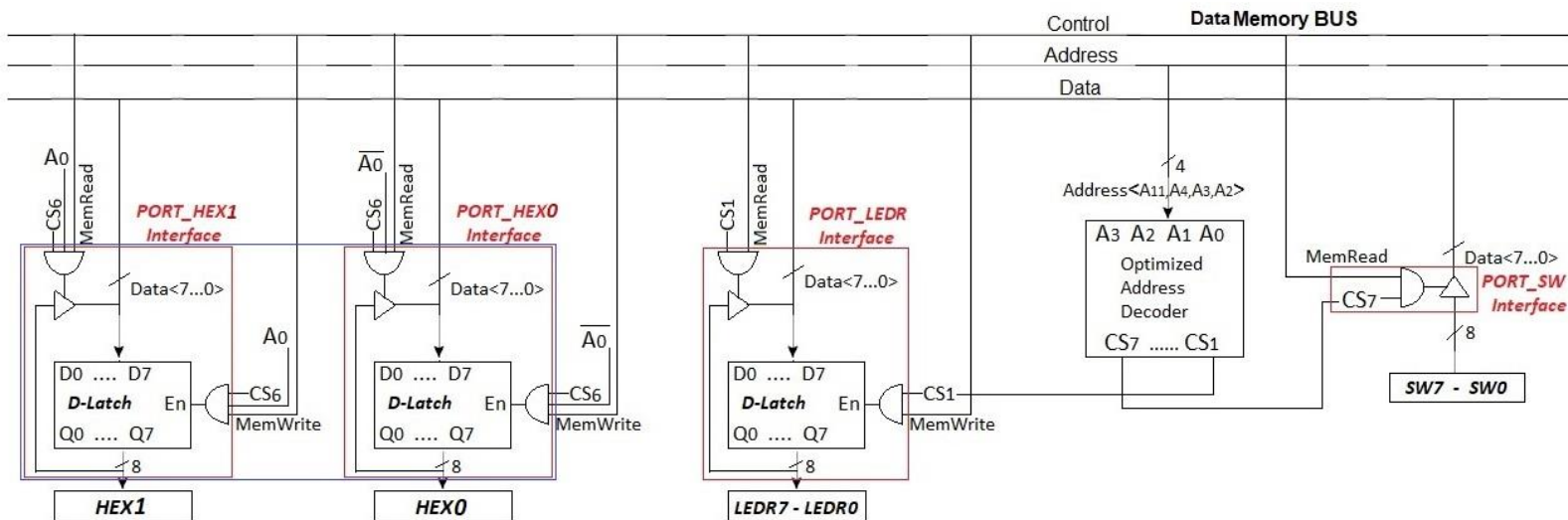


Figure 3: Primitive GPIO peripheral connection using Memory Mapped I/O approach

- The CPU will be based on the *standard 32bit MIPS ISA* and the Instructions will be 32 bit wide. The following table shows the MIPS instruction format. For more information, see MIPS technical documents [1].

| Type | -31- format (bits) -0- | | | | | |
|------|------------------------------|--------------|--------|----------------|-----------|-----------|
| R | opcode (6) | rs (5) | rt (5) | rd (5) | shamt (5) | funct (6) |
| I | opcode (6) | rs (5) | rt (5) | immediate (16) | | |
| J | opcode (6) | address (26) | | | | |

Table 1 : MIPS Instruction format


The Data address space is 4kB. Memory latency will be according to Table 2

| Memory | Write Latency | Read Latency |
|---------------------------------|---------------|--------------|
| Program Memory (I-Cache / ITCM) | 1 clk | 1 clk |
| Data Memory (D-Cache / DTCM) | 1 clk | 1 clk |


Table 2 : Memory size and latency

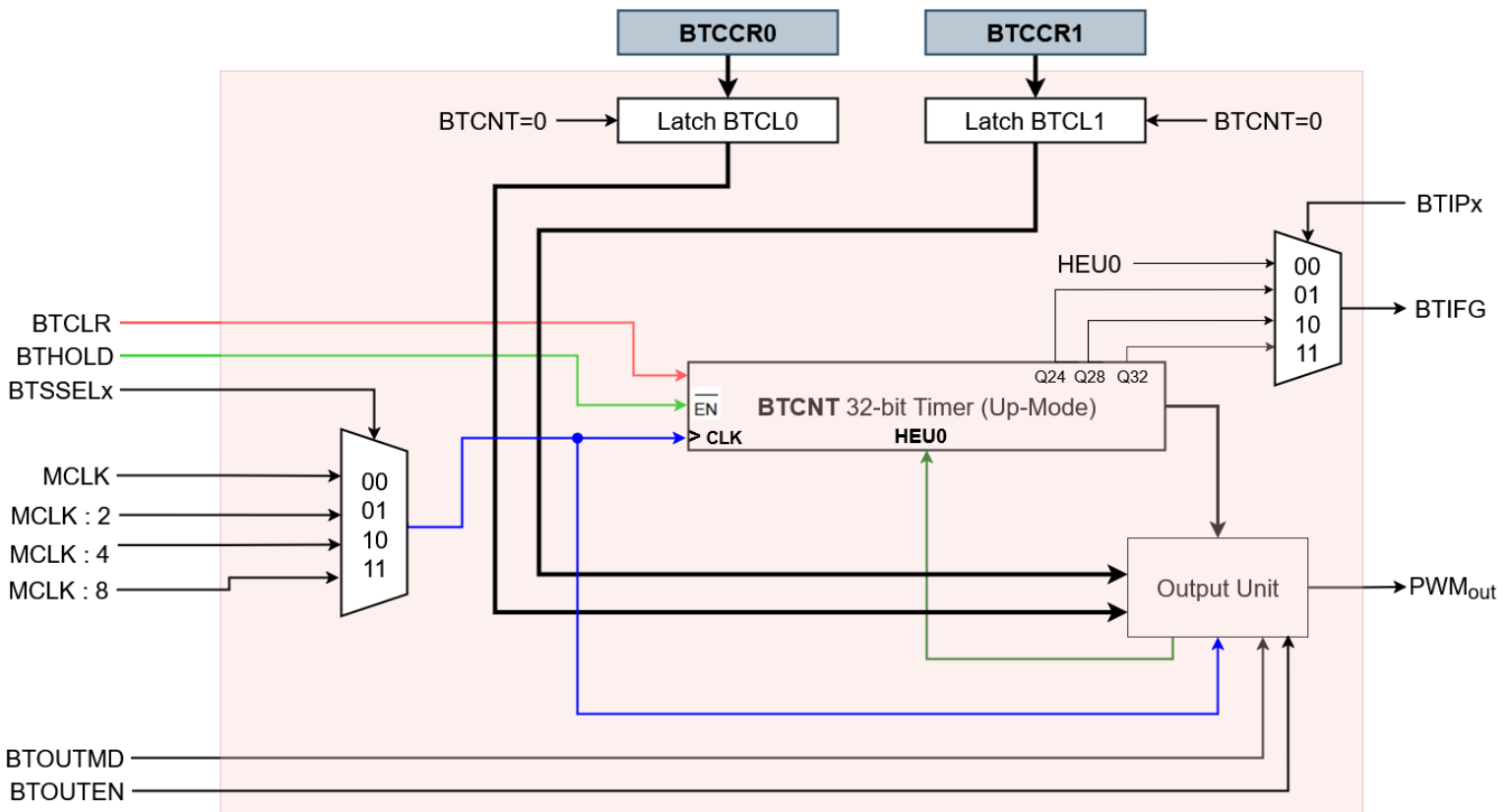4. Required Support of CPU Peripherals


- Seven GPIO ports** (six Output and one Input) for peripherals depicted in page 5
- KEY [3-1]:** support array of *three* pushbuttons as input device
- Basic Timer with output comparing capabilities:**




BTCTL, Basic Timer Control Register

 

BTCNT, Basic Timer Counter

 


BTCCR_x, Basic Timer Compare Register x

 


Basic Timer Output compare registers $x = \{0,1\}$

Compare data is written to each **BTCCR_x** and automatically transferred to **BTCL_x**. **BTCL_x** holds the data for the comparison to the timer value in the Basic Timer Register, BTCNT.

 Note: The register value is zero on RESET.




iv. FIR filter HW-Accelerator:

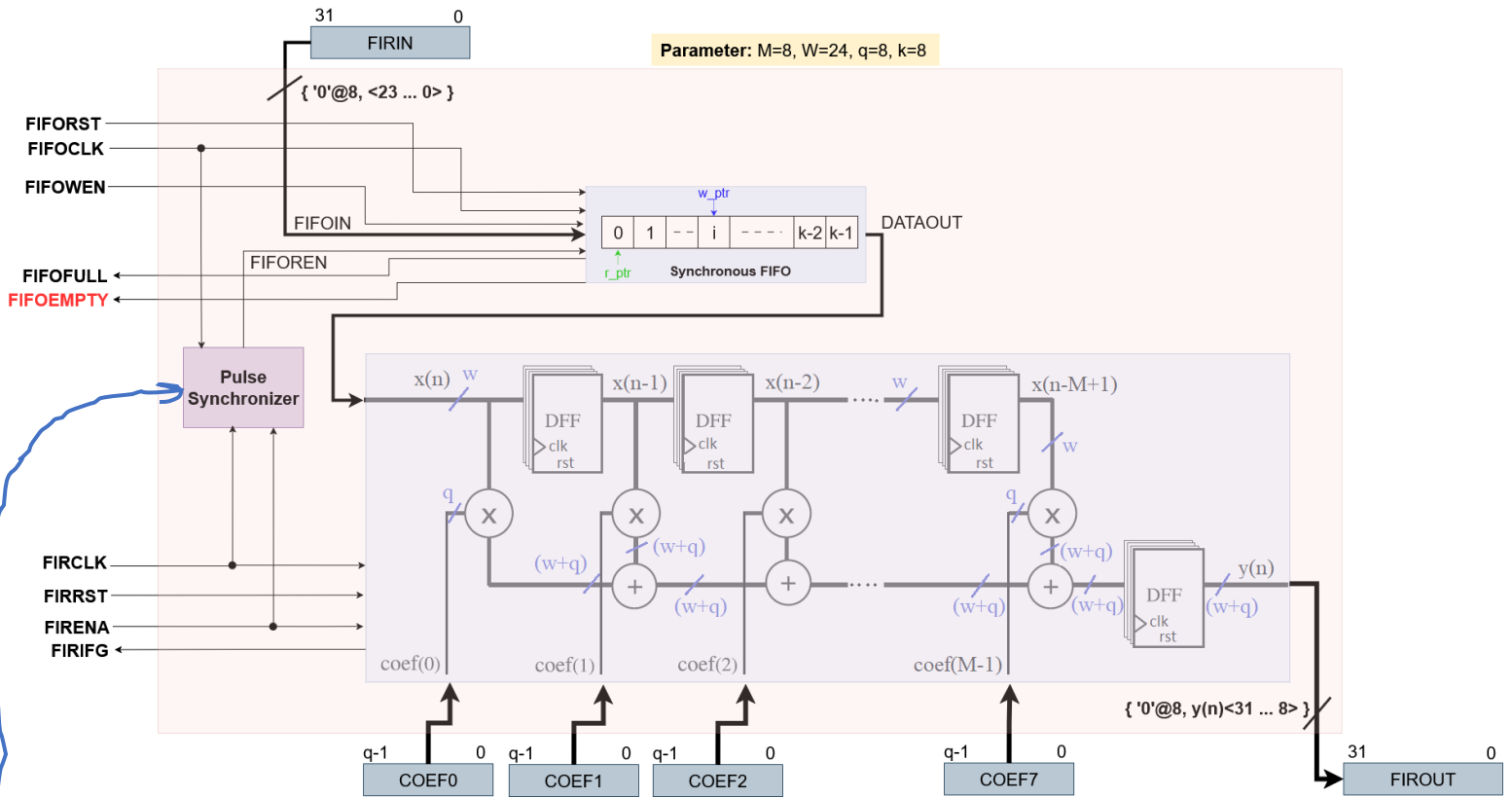


FIFOREN synchronizer functional diagram


COEFx, FIR filter coefficient x

 



FIROUT, FIR filter output data

 

FIRIN, FIR filter input data

 

FIRCTL, FIR filter control

  

v. **USART Peripheral Interface, UART Mode (Bonus 20%):**

The required communication peripheral is the universal **USART** (synchronous/asynchronous receive/transmit) peripheral interface in **UART Mode** only (degenerated **USART**).

You are given a VHDL design code that needs to be adapted to the following UART mode features.

UART mode features include:

- 1-start bit, 1-stop-bit, 8-bit data with non-parity
- Independent transmit and receive shift registers
- Separate transmit and receive buffer registers
- LSB-first data transmit and receive
- Programmable baud rate support
- Status flags for error detection
- Independent interrupt capability for receive and transmit

UCTL, USART Control Register

| | | | | | | | |
|-------------|-----------|-----------|-----------|-----------------|------------|-------------|--------------|
| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
| BUSY | OE | PE | FE | BAUDRATE | PEV | PENA | SWRST |
| r | r | r | r | rw | rw | rw | rw |

| | | |
|-----------------|-------|--|
| SWRST | Bit 0 | Software reset enable 0 Disabled. USART reset released for operation 1 Enabled. USART logic held in reset state |
| PENA | Bit 1 | Parity enable 0 Parity disabled 1 Parity enabled. Parity bit is generated (TXD) and expected (RXD). |
| PEV | Bit 2 | Parity select. PEV is not used when parity is disabled. 0 Odd parity 1 Even parity |
| BAUDRATE | Bit 3 | Baud Rate value 0 9600 1 115200 |
| FE | Bit 4 | Framing error flag 0 No error 1 Character received with low stop bit |
| PE | Bit 5 | Parity error flag. When PENA = 0, PE is read as 0. 0 No error 1 Character received with parity error |
| OE | Bit 6 | Overrun error flag. This bit is set when a character is transferred into UxRXBUF before the previous character was read. 0 No error 1 Overrun error occurred |
| BUSY | Bit 7 | This bit indicates if a transmit or receive operation is in progress (busy). 0 UART module inactive 1 UART module transmitting or receiving |

RXBUF, USART Receive Buffer Register

| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 2 ⁷ | 2 ⁶ | 2 ⁵ | 2 ⁴ | 2 ³ | 2 ² | 2 ¹ | 2 ⁰ |
| r | r | r | r | r | r | r | r |

RXBUF_x Bits 7-0 The receive-data buffer is user accessible and contains the last received character from the receive shift register. Reading RXBUF resets the receive-error bits, and RXIFG.


TXBUF, USART Transmit Buffer Register

| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 2 ⁷ | 2 ⁶ | 2 ⁵ | 2 ⁴ | 2 ³ | 2 ² | 2 ¹ | 2 ⁰ |
| rw | rw | rw | rw | rw | rw | rw | rw |

TXBUF_x Bits 7-0 The transmit data buffer is user accessible and holds the data waiting to be moved into the transmit shift register and transmitted on TXD. Writing to the transmit data buffer clears TXIFG.

Note: for UART module reference, see block diagram of MCUs that use acquainted with.


vi. Interrupt controller:

 


Notes:

- The **BTIFG** and **FIRIFG** flags are reset automatically when the interrupt is serviced.
- RXIFG** is automatically reset if the pending interrupt is served or when **RXBUF** is read.
- TXIFG** is automatically reset if the interrupt request is serviced or if a character is written to **TXBUF**
- The **KEYIFG** is reset manually with software (**BTIFG**, **DIVIFG**, **RXIFG**, **TXIFG** as well).
- As part of CPU services an interrupt, **GIE** is clear (*in HW*) means DINT of other interrupts. Symmetrically, as part of CPU returning from interrupt, **GIE** is set (*in HW*) means EINT of interrupts (back the origin state).

Handling an interrupt:

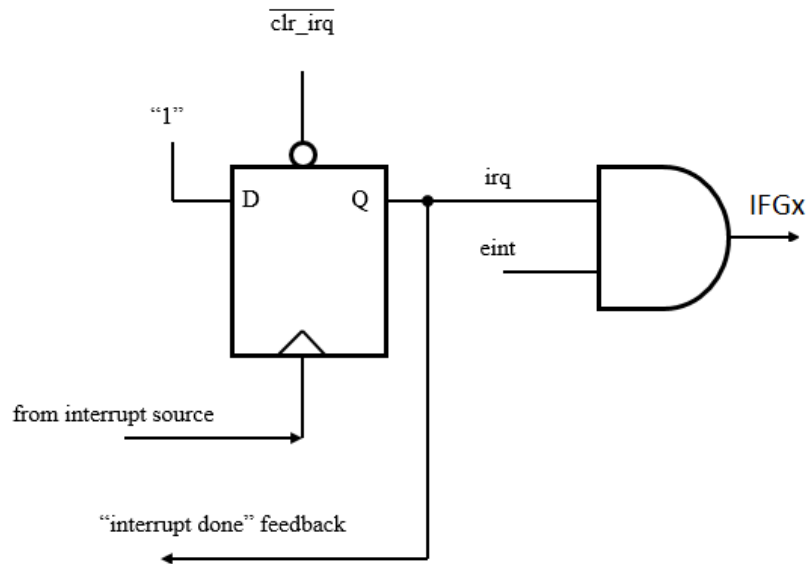

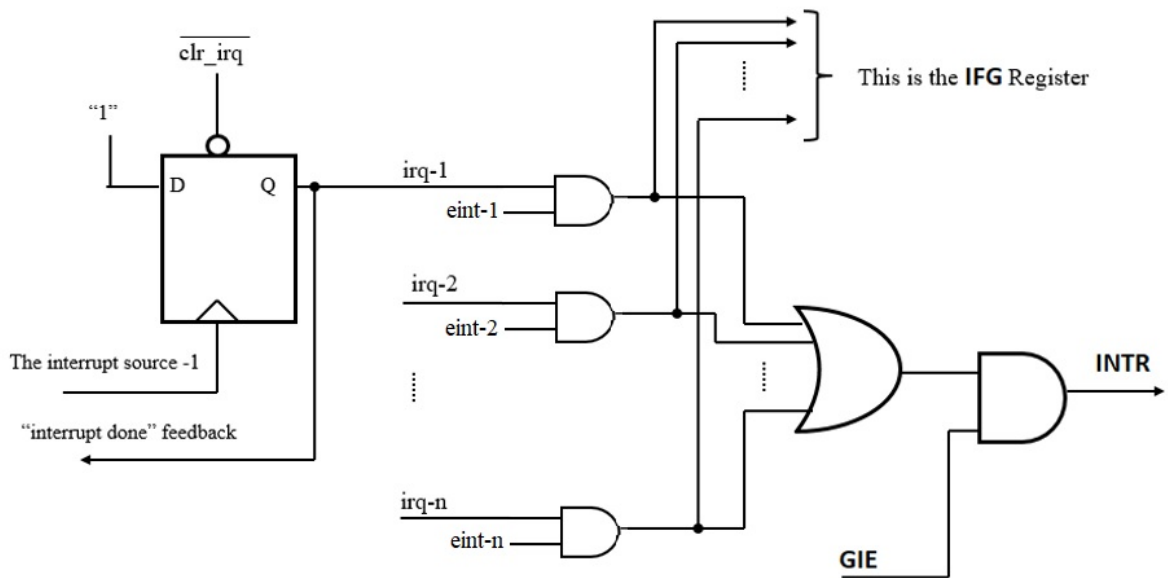Handling interrupts from several sources:



IE, Interrupt Enable Register

| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
|-----|-------|--------|--------|--------|------|------|------|
| 0 | FIRIE | KEY3IE | KEY2IE | KEY1IE | BTIE | TXIE | RXIE |
| r-0 | rw | rw | rw | rw | rw | rw | rw |


IEx Bit x 0 Interrupt not enabled
1 Interrupt enabled

IFG, Interrupt Flag Register

| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 |
|-----|--------|---------|---------|---------|-------|-------|-------|
| 0 | FIRIFG | KEY3IFG | KEY2IFG | KEY1IFG | BTIFG | TXIFG | RXIFG |
| r-0 | rw | rw | rw | rw | rw | rw | rw |

IFGx Bit x 0 No interrupt pending
1 Interrupt pending

TYPE, Interrupt Type Register

 

| TYPE Contents | Interrupt Source | Interrupt Flag | Interrupt Priority | |
|---------------|-------------------|----------------|--------------------|--------------------------|
| 00h | RESET | NMI | Highest | (Non)-Maskable Interrupt |
| 04h | UART status error | RXIFG | | |
| 08h | UART RX | | | Maskable Interrupt |
| 0Ch | UART TX | TXIFG | | |
| 10h | Basic Timer | BTIFG | | |
| 14h | KEY1 | KEY1IFG | | |
| 18h | KEY2 | KEY2IFG | | |
| 1Ch | KEY3 | KEY3IFG | | |
| 20h | FIFOEMPTY | | Lowest | |
| 24h | FIROUT | FIRIFG | | |

MEMORY Mapped I/O

```
#define PORT_LEDR[7-0] 0x800 - LSB byte (Output Mode)
#----- PORT_HEX0_HEX1 -----
#define PORT_HEX0[7-0] 0x804 - LSB byte (Output Mode)
#define PORT_HEX1[7-0] 0x805 - LSB byte (Output Mode)
#----- PORT_HEX2_HEX3 -----
#define PORT_HEX2[7-0] 0x808 - LSB byte (Output Mode)
#define PORT_HEX3[7-0] 0x809 - LSB byte (Output Mode)
#----- PORT_HEX4_HEX5 -----
#define PORT_HEX4[7-0] 0x80C - LSB byte (Output Mode)
#define PORT_HEX5[7-0] 0x80D - LSB byte (Output Mode)
#-----
#define PORT_SW[7-0] 0x810 - LSB byte (Input Mode)
```

```
#define PORT_KEY[3-1] 0x814 - LSB nibble (3 push-buttons - Input Mode)
#-----
#define UTCL 0x818 - Byte
#define RXBF 0x819 - Byte
#define TXBF 0x81A - Byte
#-----
#define BTCTL 0x81C - LSB byte
#define BTCNT 0x820 - Word
#define BTCCR0 0x824 - Word
#define BTCCR1 0x828 - Word
#-----
#define FIRCTL 0x82C - Word
#define FIRIN 0x830 - Word
#define FIROUT 0x834 - Word
#define COEF3_0 0x838 - Word
#define COEF7_4 0x83C - Word
#-----
#define IE 0x840 - LSB byte
#define IFG 0x841 - LSB byte
#define TYPE 0x842 - LSB byte
```

GPIO
without
interrupt
capability

Peripherals
with interrupt
capability

5. Interrupt Service BUS Protocol of a Single-Cycle CPU:

1. CPU services an interrupt request (latency of two or three cycles):

This ongoing event is triggered on the falling edge of an INTA signal (the ensuing cycle after INTR is set to '1')

- i.* GIE=0 (bit \$k0[0] = 0)
- ii.* Writing content of register TYPE on Data BUS
Note: cannot be written on Address BUS because CPU is the only BUS master (executes this protocol).
- iii.* Set INTA (INTA='1'), clear BTIFG, DIVIFG flags (in case they were risen)
- iv.* Serial emulation execution of **load** (of TYPE content) and **jal** (to Mem [TYPE] content) where \$k1=PC+4

2. CPU returning from service of an interrupt request (latency of one cycle):

This event happens as a part of **reti** (**jr** \$k1) execution

GIE=1 (bit \$k0[0] = 1) and go to return address stored in \$k1

6. Pin Planner

Only MCU IO devices need to be connected to FPGA location legs via pin planner. Location legs that used for proof of work phase (signal tap) need to be removed at the final step.

7. Host Interface (to ITCM and DTCM)

After the last system developing stage, you will be given a made JTAG based code wrapper of communication interface to L1 memory caches (data and program) in order to upload/download their content without reloading the system hardware design onto the FPGA chip.

8. Compiler, Simulator and Memory

The MARS compiler and simulator, or any other can be used to compile and simulate the assembly code. MARS compiler can also export the memory contents into the file in format that VHDL can easily read. It can also simulate a cache performance.

The mars compiler, installation instructions and documentation are available at: <http://courses.missouristate.edu/KenVollmar/MARS/>

9. CPU and MCU Test


- a) **Mandatory:** supporting all of given *test_i.asm* assembly source files.
- b) **Bonus (= under condition of working properly):** Using serial communication support application of PC side (as *Hyper-Terminal*, *Tera-Term*, *puTTY* etc) and write code for MCU side that support the next menu (transmitted from MCU to PC):

Menu

1. Count up from 0x00 onto LEDG with delay ~0.5sec
2. Count down from 0xFF onto LEDR with delay ~0.5sec
3. Clear all LEDs
4. On each KEY1 pressed, send the message "I love my Negev"
5. Show Menu

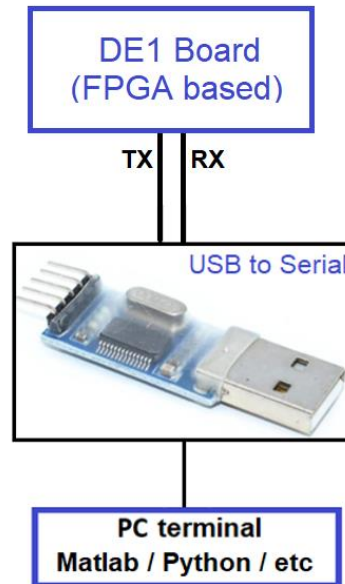10. MCU and PC communication using RS-232 interface (= Bonus)

The FTDI driver emulates a standard PC serial port such that the USB device may be communicated with as a standard RS-232 device. The driver allows direct access to a USB device via a DLL interface.



11. Requirements

You have to do the following tasks:

- ModelSim Simulation with maximal coverage.
- Analyze the critical path, explain where it is in your VHDL design and find the maximal operating clock.
- Load the design onto the FPGA and verify the simulation results.
- **Run the required assembly source codes and explore them.**

The following must be presented in **final.pdf** report file.

1. Top level block review diagram of your design.
2. For each block in the top level design:
 - RTL Viewer results
 - Logic usage for each block (Combinational and Flip-Flops).
 - Graphical description (a square with ports going in and out).
 - Port Table (direction, size, functionality).
 - Short description.

3. Maximum (Critical) path of your design – explain where it is in the code and how it is possible to optimize if you would have more time. What is the maximum clock frequency?
4. Minimum path analysis.
5. Documentation Style - Content with page numbers, Images and tables will be numbered. The caption of an images and tables below the images or tables.
6. Elaborated analysis and wave forms:
 - Maximal Frequency and critical paths from Timing Analyzer.
 - Proof of work using Signal Tap shot screens.
Recall that, proof of work using Signal Tap is mandatory.
 - **One** basic waveform to explain the system timing.

Design requirements:

1. The design must be well commented.
2. The system must work from only one clock.
3. System RESET (KEY0) must be synchronous.
4. Conclusions
5. A ZIP file in the form of **id1_id2.zip** (where id1 and id2 are the identification number of the submitters, and id1 < id2) *must be upload to Moodle only by student with id1* (any of these rules violation disqualifies the task submission).
6. The **ZIP** file will contain the next six subdirectories (*only the exact next sub folders*):

| Directory | Contains | Comments |
|-----------|---|---|
| DUT | Project VHDL / Verilog HDL files (you must use only a single version of DUT files which are adapted to ModelSim and Quartus IDEs under method of conditional compilation using generic map of Boolean parameter) | Only VHDL / Verilog HDL files, excluding test bench Note: your project files must be well compiled (in ModelSim and Quartus separately) without errors as a basic condition before submission |
| TB | VHDL files that are used for test bench | Only one tb.vhd for the overall DUT |
| SIM | ModelSim DO files | Only for tb.vhd of the overall DUT |
| DOC | Project documentation | Readme.txt and final.pdf full report file |
| Quartus | <ul style="list-style-type: none"> • Signal Tap files used in project verification • Project SOF file • Project SDC file | Do not place files that are not relevant for compilation or is a result of compilation! |
| CODE | The assembly source code of clause 6b | |

Table 3 : Directory Structure

12. Grading policy

| Weight | Task | Description |
|--------|-------------------------------------|--|
| 10% | Full Documentation | The "clear" way in which you presented the requirements and the analysis and conclusions on the work you've done |
| 90% | System Execution, Analysis and Test | The correct analysis of the system (under the requirements) |

Table 4: Grading

Late submissions will be not gotten.

13. References

[1]. MIPS32® Architecture for Programmers Volume I to III (from Moodle under Final Project)

[2]. ALTPLL User Guide: http://www.altera.com/literature/ug/ug_altpll.pdf

[3]. Altera RAM user guide: http://www.altera.com/literature/ug/ug_ram_rom.pdf

[4]. Altera MegaFunction User Guide:

www.altera.com/literature/ug/ug_intro_to_megafunctions.pdf

[5]. Bin2Hex utility

32bit - <http://www.keil.com/download/docs/113.asp>

64bit - <http://www.ht-lab.com/freeutils/bin2hex/bin2hex.html>